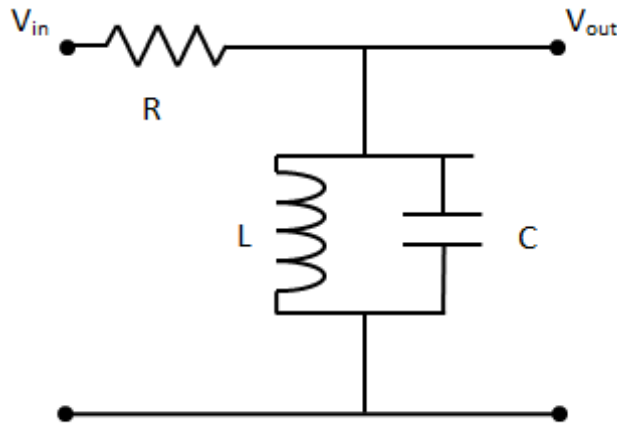


Bandpass Filter Design



The product LC controls the bandpass frequency while RC controls how narrow the passing band is. To build a bandpass filter tuned to 1 rad/s , set $L = C = 1$ and use R to tune the filter band.

Use functions from
DynamicSystems package

```
DF := DynamicSystems
```

Response of a bandpass
filter


$$G := \frac{\frac{s}{R \cdot C}}{s^2 + \frac{s}{R \cdot C} + \frac{1}{L \cdot C}}$$

Transfer function object

```
TF := DF:-TransferFunction(G)
```

Magnitude plot
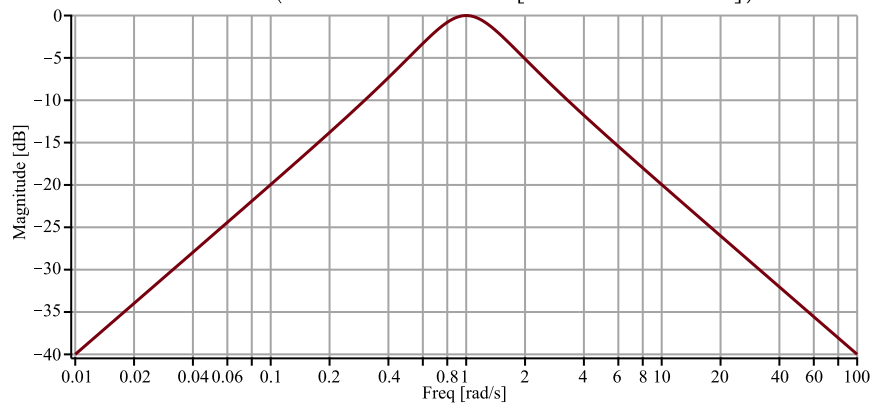
```
DF:-MagnitudePlot(TF, parameters = [R = 1, L = 1, C = 1]) =
```




As expected, the RLC filter has maximum gain at the frequency 1 rad/s . However the attenuation is only -10 dB away from this frequency.

Get a narrower passing band
by increasing R

$$R_f := 100$$
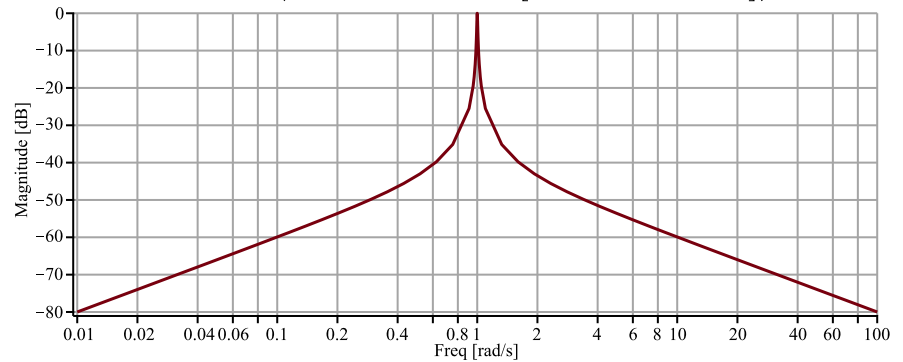
```
DF: -MagnitudePlot(TF, parameters = [R = R_f, L = 1, C = 1]) =
```



The resistor value $R = 20$ gives a filter narrowly tuned around the target frequency of 1 rad/s

We can confirm the attenuation properties of the circuit by simulating how this filter transforms sine waves.

Frequencies $f_1 := 0.9$ $f_2 := 1$

```
p1 := DF: -ResponsePlot(TF, sin(f_1 * t), duration = 100, parameters = [R = R_f, L = 1, C = 1],  
color = "DarkRed", thickness = 1, legend = sprintf("%.2f rad/s", f_1))
```

```
p2 := DF: -ResponsePlot(TF, sin(f_2 * t), duration = 100, parameters = [R = R_f, L = 1, C = 1],  
color = "Nautical Light Blue", thickness = 1, legend = sprintf("%.2f rad/s", f_2))
```

```
plots: -display(p1, p2, axes = box) =
```

