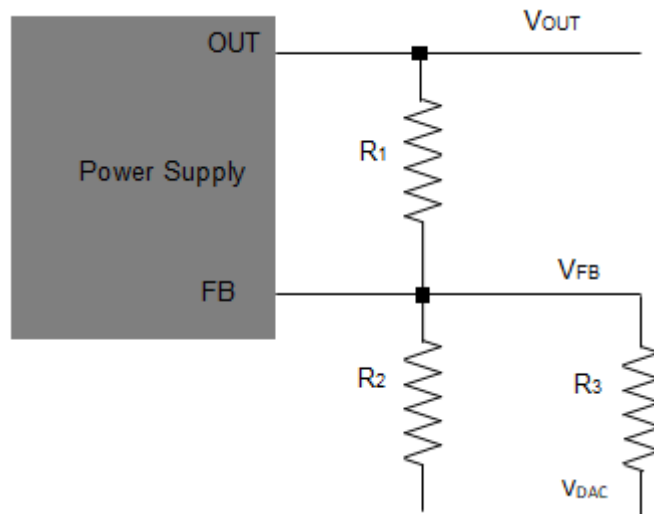


Variable Voltage Power Supply Control Input

This application will calculate the resistances R_1 and R_3 for this power supply.



Circuit equation

$$\text{circuit} := \frac{V_{\text{OUT}} - V_{\text{FB}}}{R_1} + \frac{V_{\text{DAC}} - V_{\text{FB}}}{R_3} - \frac{V_{\text{FB}}}{R_2} = 0 \text{ A}$$

Solve for V_{OUT}

$$V_{\text{OUT}} := \text{solve}(\text{circuit}, V_{\text{OUT}})$$

$$V_{\text{OUT}} = - \frac{R_1 \cdot R_2 \cdot V_{\text{DAC}} - R_1 \cdot R_2 \cdot V_{\text{FB}} - V_{\text{FB}} \cdot R_1 \cdot R_3 - R_2 \cdot R_3 \cdot V_{\text{FB}}}{R_3 \cdot R_2}$$

Highest and lowest desired power supply voltage

$$V_{\text{high}} := 60 \text{ V}$$

$$V_{\text{low}} := 20 \text{ V}$$

DAC voltage for maximum and minimum power supply voltage

$$V_{\text{DAC_low}} := 0 \text{ V}$$

$$V_{\text{DAC_high}} := 2.5 \text{ V}$$

Feedback voltage that power supply tries to maintain

$$V_{\text{FB}} := 2.7 \text{ V}$$

One resistor must be selected arbitrarily

$$R_2 := 8 \times 10^3 \Omega$$

Solve for R_1 and R_3

$$\text{sol} := \text{fsolve}\left(\left\{\begin{array}{l} \text{eval}\left(V_{\text{OUT}}, V_{\text{DAC}} = V_{\text{DAC_high}}\right) = V_{\text{low}} \\ \text{eval}\left(V_{\text{OUT}}, V_{\text{DAC}} = V_{\text{DAC_low}}\right) = V_{\text{high}} \end{array}\right\}, \left\{R_1 = 300 \times 10^3 \text{ ohm}, R_3 = 20 \times 10^3 \text{ ohm}\right\}\right)$$

$$\text{sol} = \left\{R_1 = 4.178 \times 10^4 \Omega, R_3 = 2.611 \times 10^3 \Omega\right\}$$